
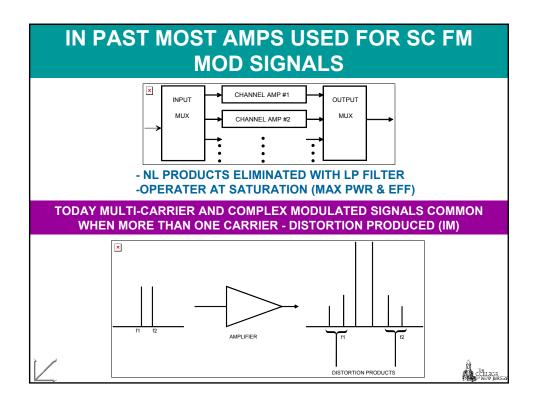



OUTLINE

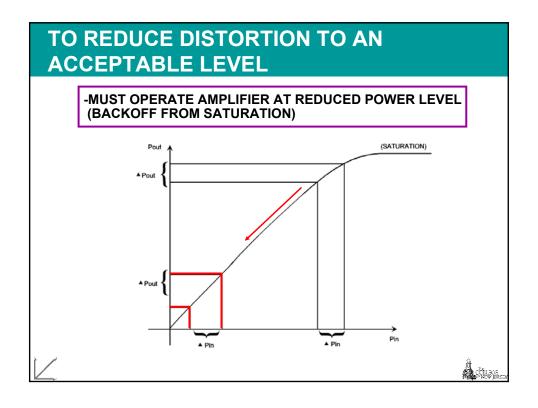
- WHY LINEARIZE
- TYPES OF LINEARIZERS
- THEORY/IDEAL LIMITER
- PREDISTORTION LINEARIZERS
- PERFORMANCE EVALUATION
- RESULTS
- CONCLUSIONS







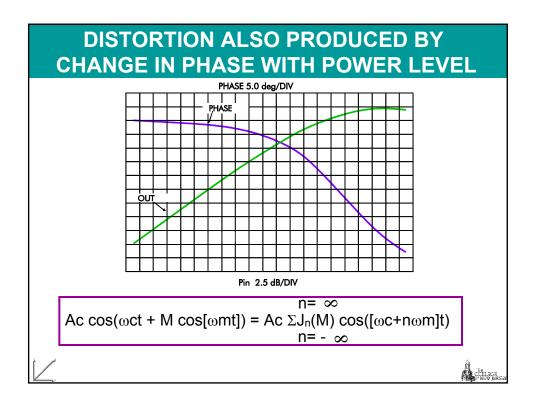

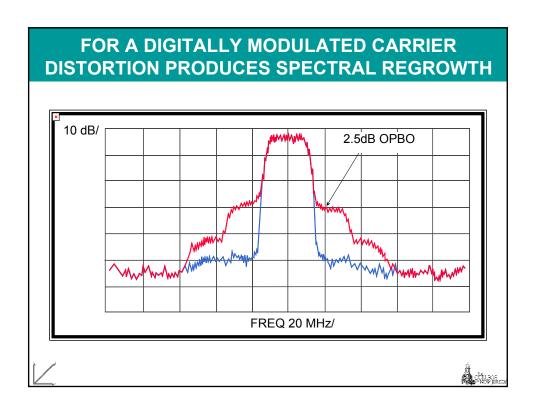

LINEARIZATION --

SYSTEMATIC PROCEDURE FOR REDUCING DISTORTIONS

USUALLY EXTRA COMPONENTS ADDED TO AN AMPLIFIER

WHEN CONFIGURED IN A SUBASSMBLY OR *BOX* KNOWN AS A **LINEARIZER**

THREE COMMON FORMS:

- 1) FEEDFORWARD
- 2) FEEDBACK
- 3) PREDISTORTION
- + TECHNIQUES TO IMPROVE EFFICIENCY USING NL PAS



CHOICE OF LINEARIZATION


- LEVEL OF LINEARITY (DISTORTION REDUCTION) NEEDED.
- BANDWIDTH REQUIRED (SIGNAL AND OPERATIONAL).
- COST/COMPLEXITY CONSTRAINTS.



LINEARIZERS HAVE BEEN USED WITH

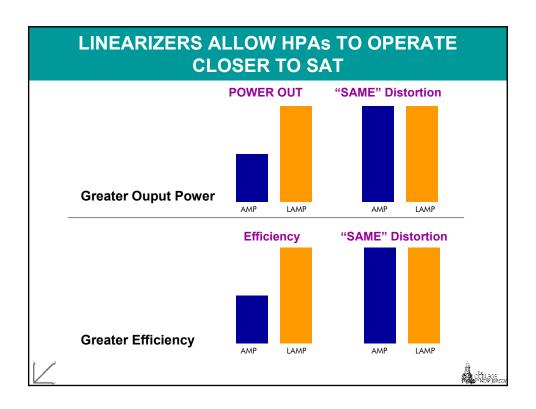- •TWTAs and KLYSTRONS
- BIPOLAR SSPAs (CLASS A, AB, B)
- •FET SSPAs (GaAs, MOS, LDMOS)





FIRST RULE:

YOU CAN'T LINEARIZE AN AMPLIFIER THAT IS ALREADY LINEAR!

WANT TO OPTIMIZE EFFICIENCY AND SATURATED POWER, NOT LINEARITY

EXCELLENT RESULTS CAN BE OBTAINED WITH CLASS A-B AND B AMPS BOTH FET AND BIPOLAR



IDEAL AMPLIFIER CHARACTERISTIC Pout Pin WANT CONSTANT GAIN AND PHASE

IMPROVEMENT DEPENDS ON ACCEPTABLE DIST LEVEL

SATELLITE --

•IMD PRODUCTS ADD TO THERMAL NOISE IF C/I = CNR THEN CNR DEGRADES BY 3 dB

•WANT C/I > CNR + 10 dB FOR NEGLIGIBLE DEG. (< .5 dB) IF CNR = 16 dB THEN C/I = 26 dB

•IF C/I = CNR + 6 THEN CNR = CNR DEG. BY 1 dB


CELLULAR --

•INTERFERENCE FROM TX TO ADJACENT RX A PROBLEM --CAN NEED C/I > 35 ~ 70 dB.

•FOR DIGITAL MOD, 16QAM ... 8PSK NEED HIGH C/I TO KEEP BER DOWN.



FEEDFORWARD

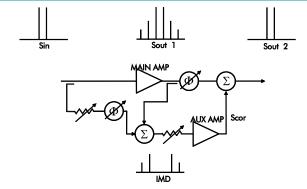

•RELATIVELY COMPLEX

•NOT WORKABLE AS STAND-ALONE UNIT


•NOT EFFECTIVE FOR OPBOs < 6 dB


•MOST USEFUL FOR VERY HIGH LINEARITY APPLICATIONS



MINIMUM FEEDFORWARD OPBO FOR IMD CANCELATION (20 dB) | Solution |

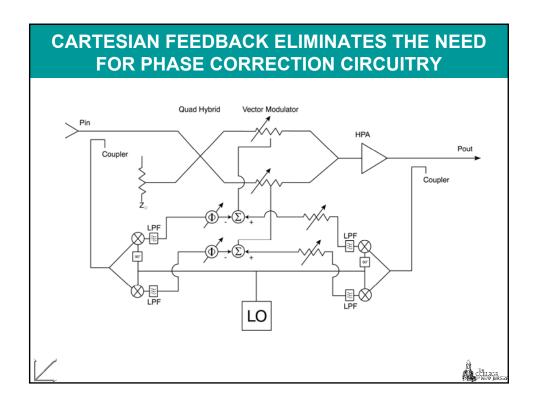*FEEDBACK (NETWORK) - NARROW BAND - STABILITY PROB - REDUCED GAIN - DIFF TO ADJ *INDIRECT FEEDBACK - OPERATES ON ENVELOPE - VERY LIMITED BW < 1/(4\Delta t_s)) - CAN BE POLAR OR CARTESIAN



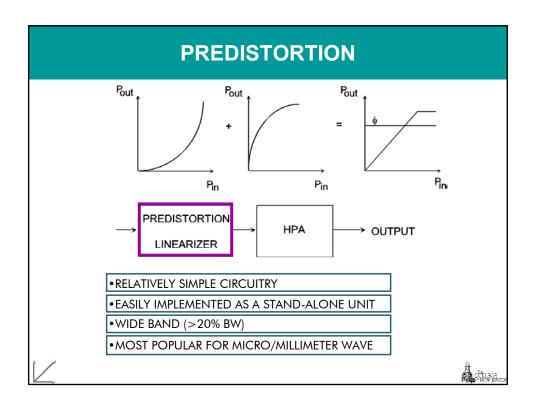

LINEARIZER GAIN DEPENDS ON INPUT TO HPA

 THE GAIN OF THE LINEARIZER (GL) MUST INCREASE BY THE SAME AMOUNT THE HPA'S GAIN (GA) DECREASES.

•
$$GL(P_{outL}) - GL_{ss} = -[GA(P_{inA}) - GA_{ss}] | P_{outL} = P_{inA}$$

•
$$\Phi L(P_{outL}) - \Phi L_{ss} = - [\Phi A(P_{inA}) - \Phi A_{ss}] | P_{outL} = P_{inA}$$


•
$$GL(P_{inL}) = GL_{ss} + GA_{ss} - GA(P_{inL} + GL(P_{inL}))$$

•
$$\Phi L(P_{inL}) = \Phi L_{ss} + \Phi A_{ss} - \Phi A(P_{inL} + GL(P_{inL}))$$

• **QL DEPENDS ON THE GL AND CANNOT BE SET IDENPENDENTLY**




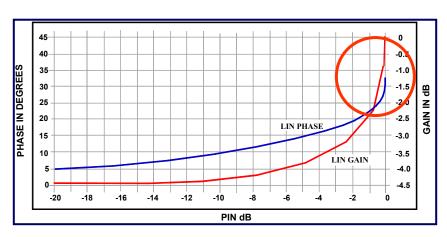AN IDEAL LINEARIZER MUST PROVIDE A GAIN EXPANSION THAT APPROACHES INFINITY NEAR SATURATION



 $dG/dP => \infty$ as Pin => Sat



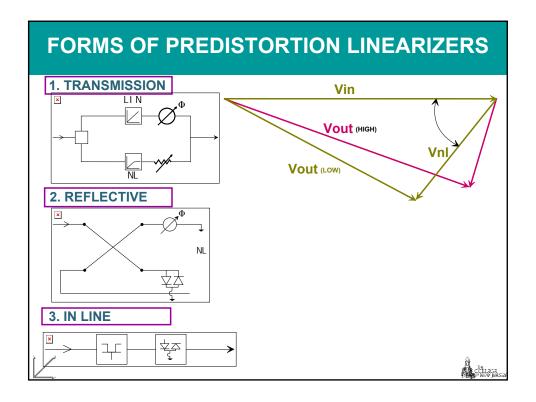


TECHNIQUES TO IMPROVE EFFICIENCY USING NL PAs

- MANY WAYS TO ACCOMPLISH.
- CLASSICAL "KHAN METHOD" DEMODS ENVELOPE AND LIMITS SIGNAL. THEN REMODULATES AT OUTPUT PA.
- LINC SYSTEMS USE OBTAIN LINEAR AMPLIFICATION BY COMBINING TWO NON-LINEAR PAS.
- LOAD MODULATION AND OUTPHASING (DOHERTY – ONE EXAMPLE)



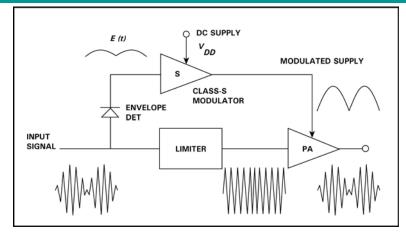
EER – ENVELOPE ELIMINATION AND RESTORATION



IF ELIMINATE ENVELOPE, SIGNAL CAN BE AMPLIFIED IN NL PA OPERATED AT OR NEAR SATURATION.



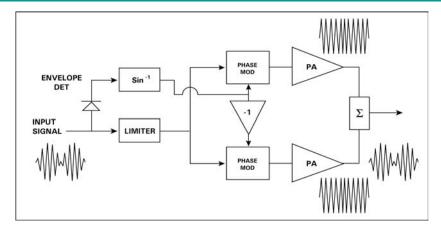LINC – LINEAR AMPLIFICATION WITH NON-LINEAR COMPONENTS




CAN OBTAIN ANY AMPLITUDE FROM THE SUM OF 2 CONSTANT AMPLITUDE SIGNALS OF VARIABLE PHASE



DIGITAL PREDISTORTION IF **MIX DOWN TO BB** MIX UP TO IF RF X (R) SIGNAL IY+QX T= sampling period • CAN PRODUCE CURVES OF ANY SHAPE NORMALLY PROCESS AT BASEBAND • CAN USE EITHER G AND Φ OR I AND Q • MUST SAMPLE AT > 2 X CORRECTION BW FOR G AND Φ • BUT ONLY > CORRECTION BW FOR I AND Q • CORRECTION BW (CBW) ≥ 3 x BW OF SIGNAL • MUST USE MANY BITS FOR HIGH CANCELATION (<6 dB/)

citizes.

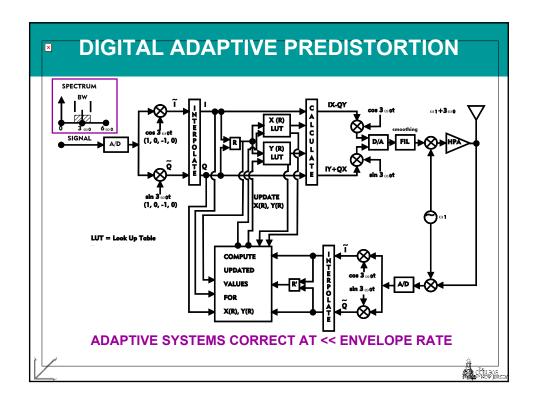

DIGITAL PREDISTORTION

ADVANTAGES:

- * ACCURATE CORRECTION OVER WIDE DYNAMIC RANGE AND FOR IRREGULAR NON MONOTONIC CHARACTERISTICS
- * EASY TO MODIFY AND UPDATE
- * SIMPLE TO IMPLEMENT AS ADAPTIVE SYSTEM

DISADVANTAGES:

- * CORRECTION BANDWIDTH LIMITED BY SAMPLING RATE: SR = CBW = N X BW
- * COST CAN BE HIGHER THAN ANALOG
- * POWER CONSUMPTION CAN BE HIGH
- * WIDE BW SYSTEMS DIFFICULT TO IMPLEMENT



PERFORMANCE EVALUATION MAGNITUDE & PHASE IMPORTANT INDICATORS OF PERFORMANCE ** OBTAIN WITH POWER SWEEP GAIN 0.5 dB/DIV Pout 2.5 dB/DIV Pin 2.5 dB/DIV Pin 2.5 dB/DIV Pin 2.5 dB/DIV SEPARATION OF 1 dB COMPRESSION AND SATURATION PROVIDES GAGE FOR COMPARISON


C/I (CARRIER TO IMD) MEASUREMENT

- MANY DIFFERENT STANDARDS MAKE COMPARISON DIF.
- DATA USUALLY PRESENTED REL TO BACKOFF FROM SAT.
- SAT POINT SHOULD BE SINGLE CARRIER SAT.
 2 CARRIER SAT ABT 1 dB LOWER, NOISE ABT 1.5 dB.
- CAN NOT USE COMPRESSION POINT FOR REFERENCE. 1 dB = SAT - D
- \bullet BOTH IPBO AND OPBO USED ... IPBO CAN BE MISLEADING. BEST TO REFER TO OPBO
 - OUTPUT LEVEL IS WHAT'S IMPORTANT!



OFTEN RESULTS PRESENTED FOR C/I3 ONLY

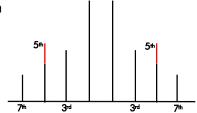With Linearizers, not uncommon for 5th order terms to be greater than 3rds or of same order





C/I total = C/ Σ / I3 ² + I5 ² + I7 ² + ...


Total C/I preferred to C/I3


C/Imin is a good compromise




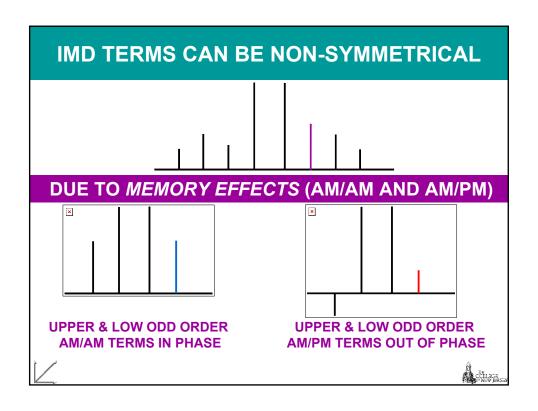


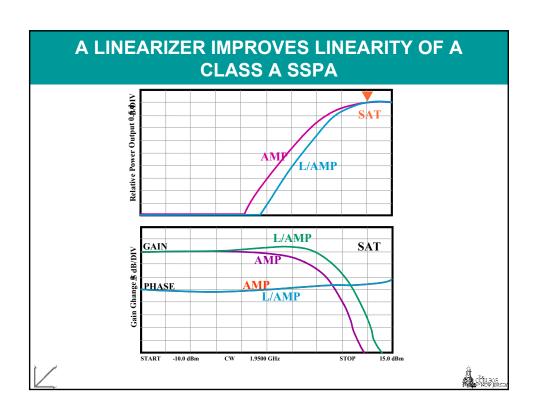


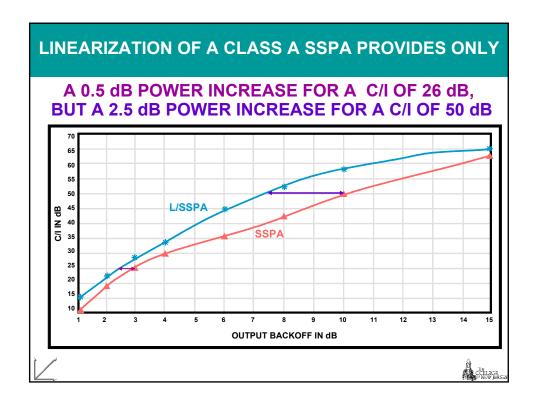


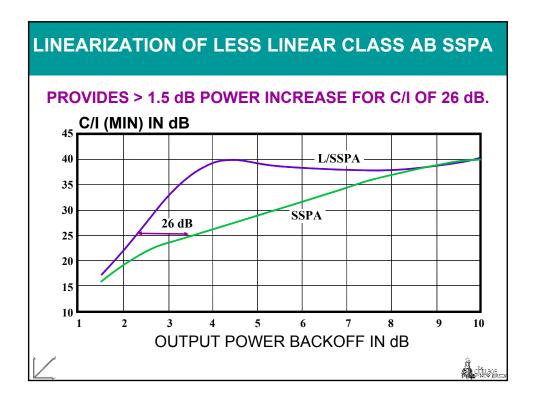


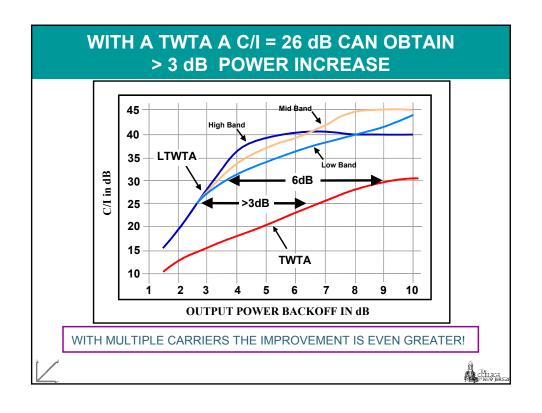


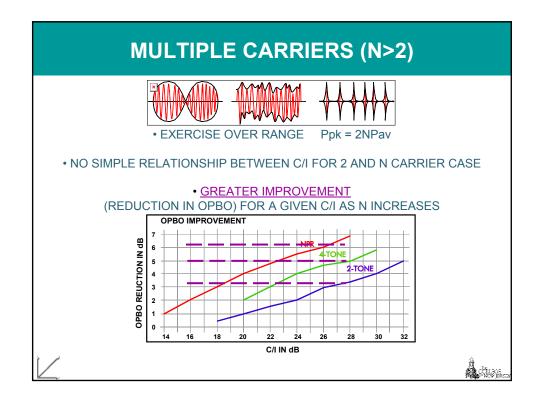


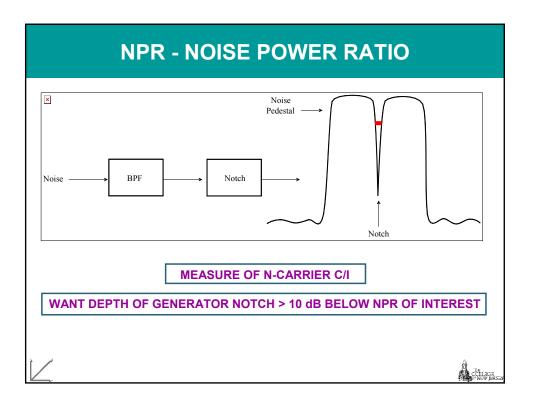


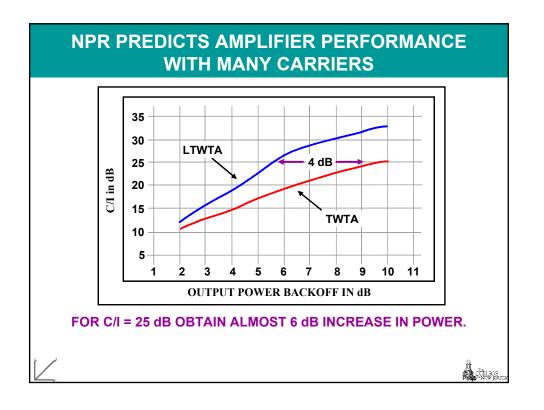


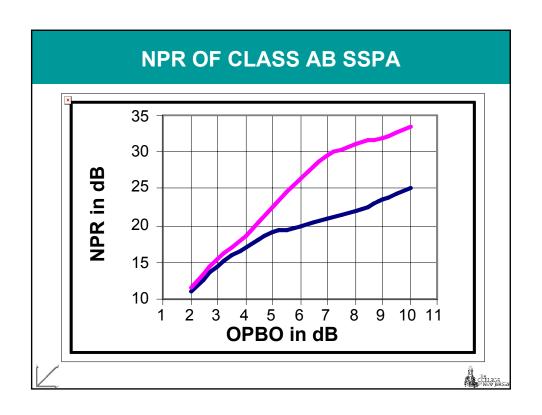


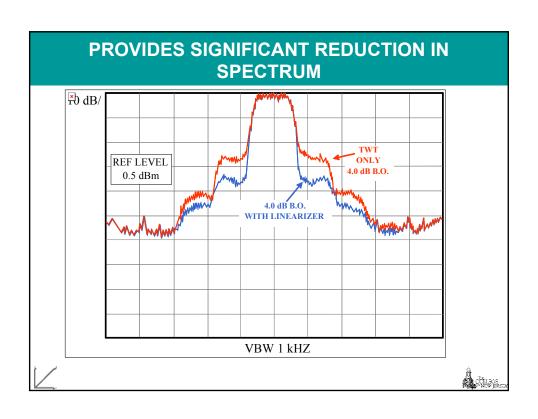


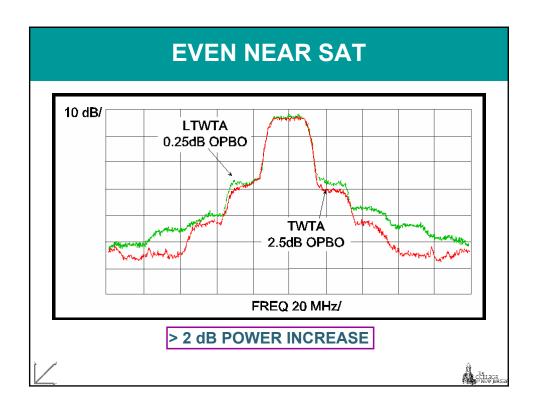


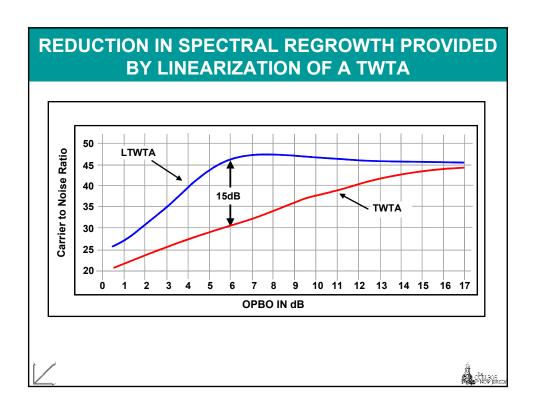


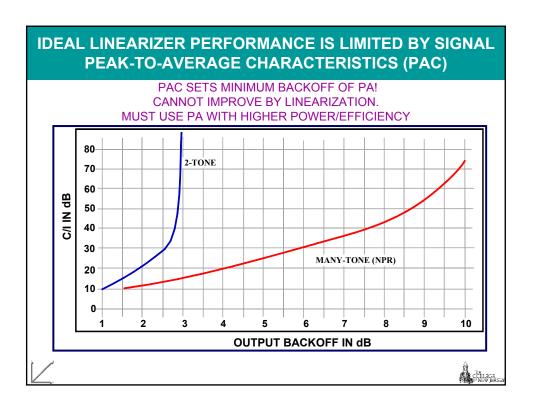

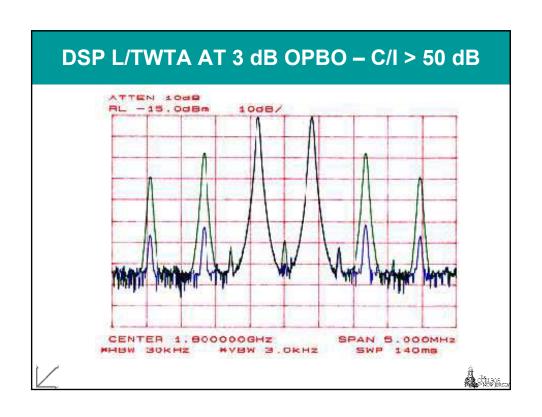

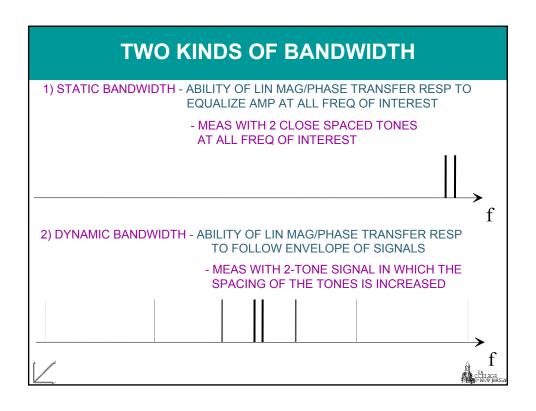

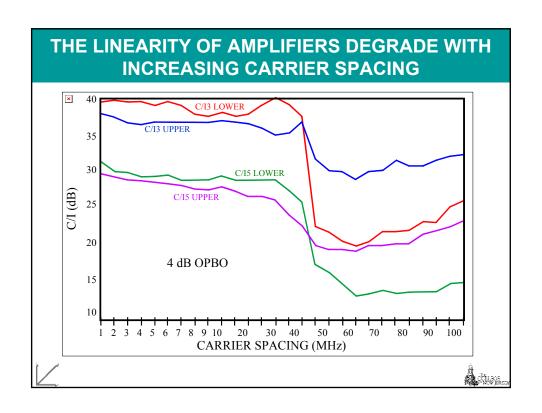

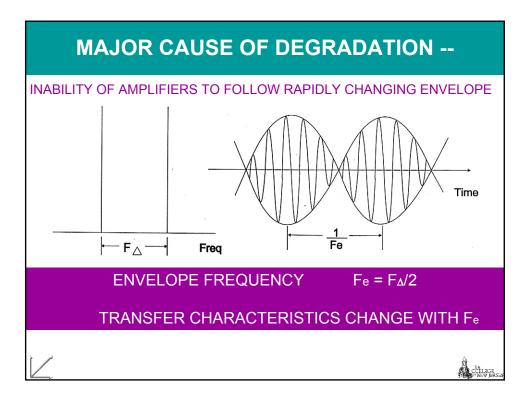


MEMORY EFFECTS

 Memory Effects are changes in a Power Amplifier's (PA) non-linear characteristics resulting from the past history of the input signal.

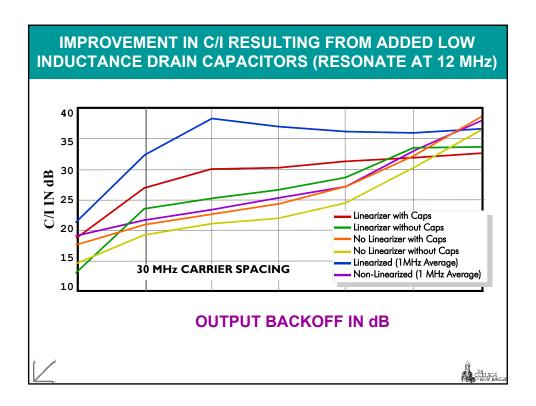- · Primary cause drain/collector and gate/base bias change.
- Thermal, device and frequency are also factors.
- Standard predistortion linearizers depend on a stable non-linear response, and can be particularly degraded by memory effects.





SUMMARY

LINEARIZERS INCREASE HPA POWER CAPACITY AND EFFICIENCY FOR MULTI-CARRIER AND COMPLEX DIGITAL SIGNALS

NEW LINEARIZER DESIGNS HAVE GREATLY ENHANCED PERFORMANCE

SSPAs - BENEFIT GREATEST FOR CLASS B AND AB 2 X POWER INCREASE IN HIGH LIN APPLICATIONS

TWTAS - 4 X POWER INCREASE AND DOUBLE EFFICIENCY



SUMMARY

FEEDFORWARD:

LINEARIZATION IS MOST VALUABLE WHEN VERY HIGH LIN REQUIRED.

INDIRECT FEEDBACK:

WORKS WELL, BUT LIMITED IN BANDWIDTH.

PREDISTORTION:

ADVANTAGES SIMPLICITY, WIDEBAND, VIABLE BOTH LOW AND HIGH LIN. DSP CAN PROVIDE VERY HIGH LIN.



FOR MORE INFORMATION

- 1. A. Katz, "Linearization: Reducing Distortion in Power Amplifiers," IEEE Microwave Magazine, pp. 37-49, December 2001.
- 2. Vuolevi and Rahkonen, "Distortion in RF Power Amplifiers", Artech House, 2003.
- 3. S. Cripps, "Advanced Techniques in RF Power Amplifier Design", Artech House, 2002.
- 4. A. Katz and R. Gray, "The Linearized Microwave Power Module," MTT-S International Microwave Symposium Digest, June, 2003.
- 5. A. Katz, "Performance Of Multi-carrier 16QAM Over a Linearized TWTA Satellite Channel," AIAA 20th International Communications Satellite Systems Conference Proceedings, Montreal, May 2002.
- 6. P. Kenington, "Methods Linearize RF Transmitters and Power Amps, Part 1, "Microwaves & RF Magazine," pp. 103-116, December 1998, Part 2, pp. 79-89, January 1999.

